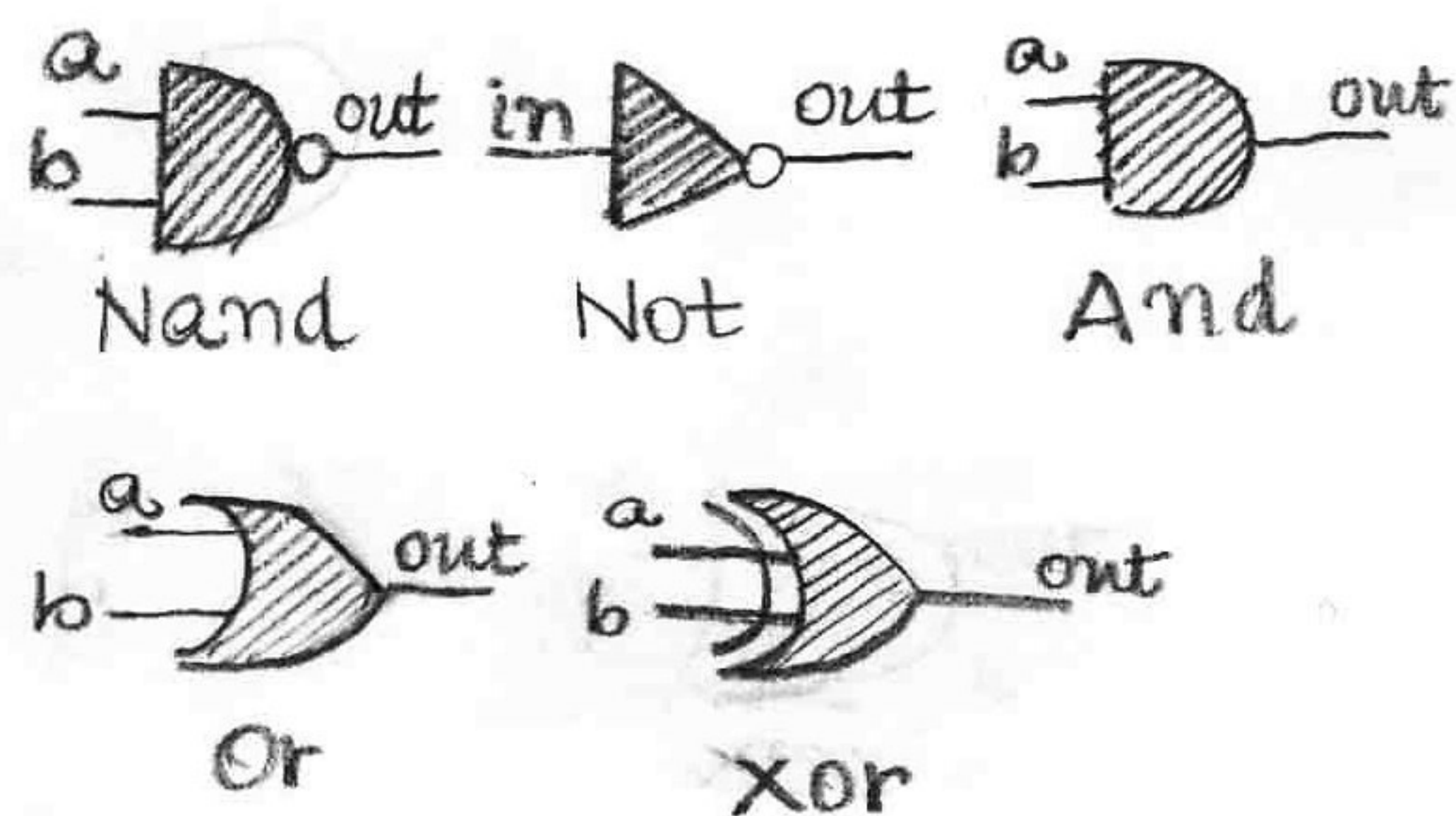


# Legend:



## Homework 01


## CS 220 - Computer Architecture + Machine Language

Author: Reesha Rajen

Section: 2653 M/W 3:30 PM-5:20 PM

Date Created: Jan. 29th 2018

### Not gate

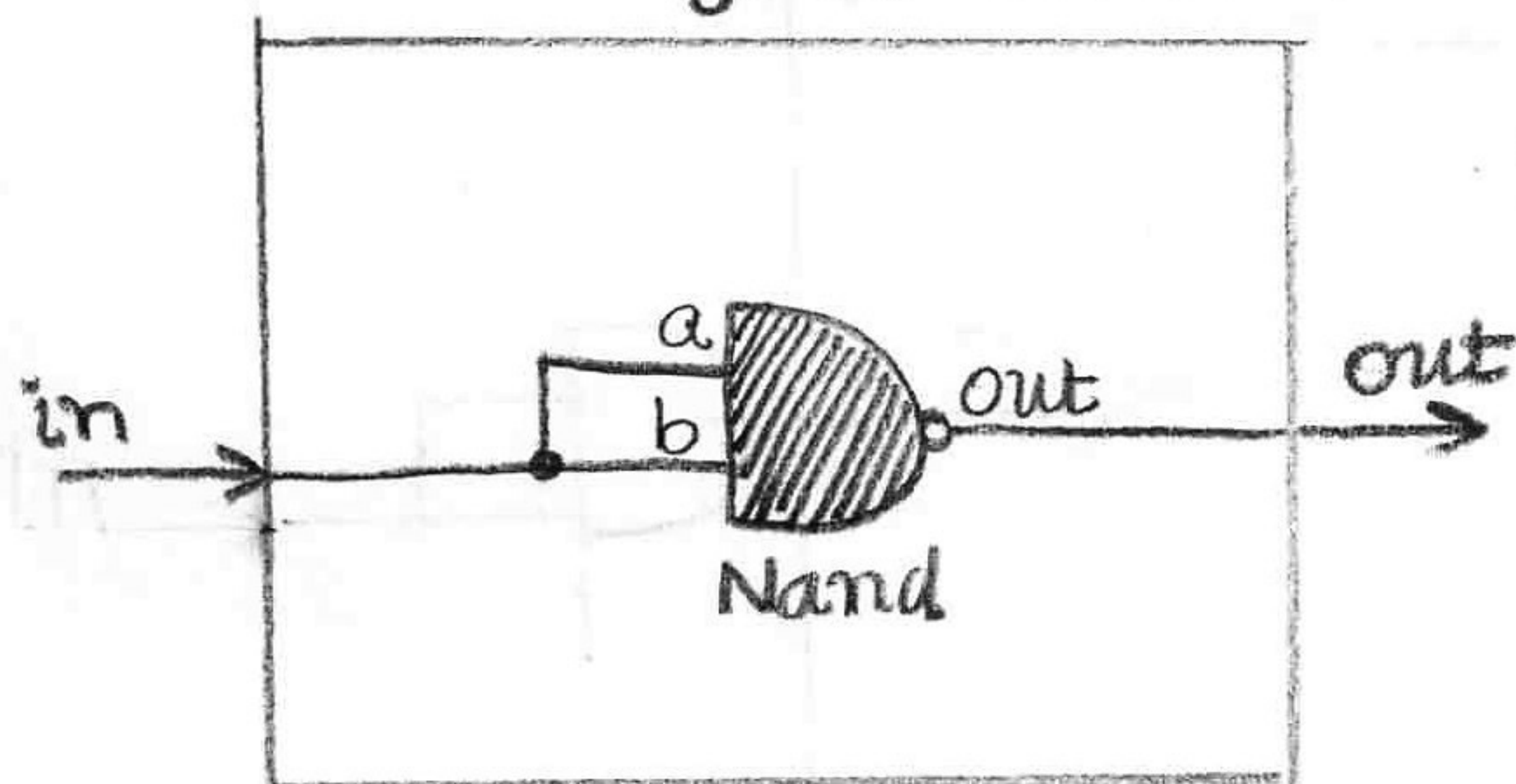

input-output

1	0
0	1

$$\text{Not}(a) = \text{Nand}(a, a)$$


Not {

IN in;  
OUT out;

Nand(a=in, b=in, out=out);

}

### And gate

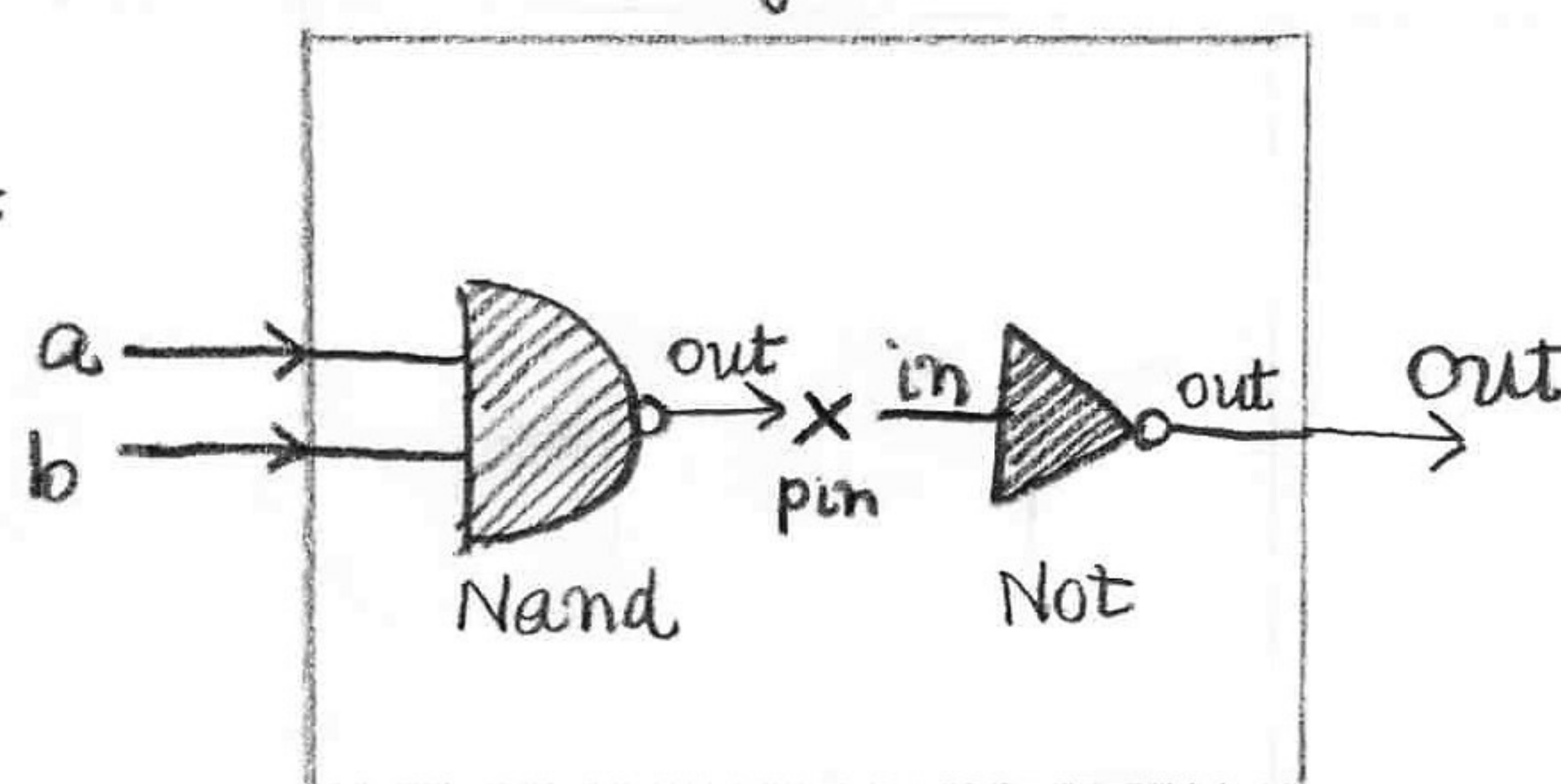

input - output

0	0	0
1	0	0
0	1	0
1	1	1

$$\text{And}(a, b) = \text{Not}(\text{Nand}(a, b))$$

And {


IN a, b;  
OUT out;

Nand(a=a, b=b, out=x);

Not(in=x, out=out);

}

### Or gate

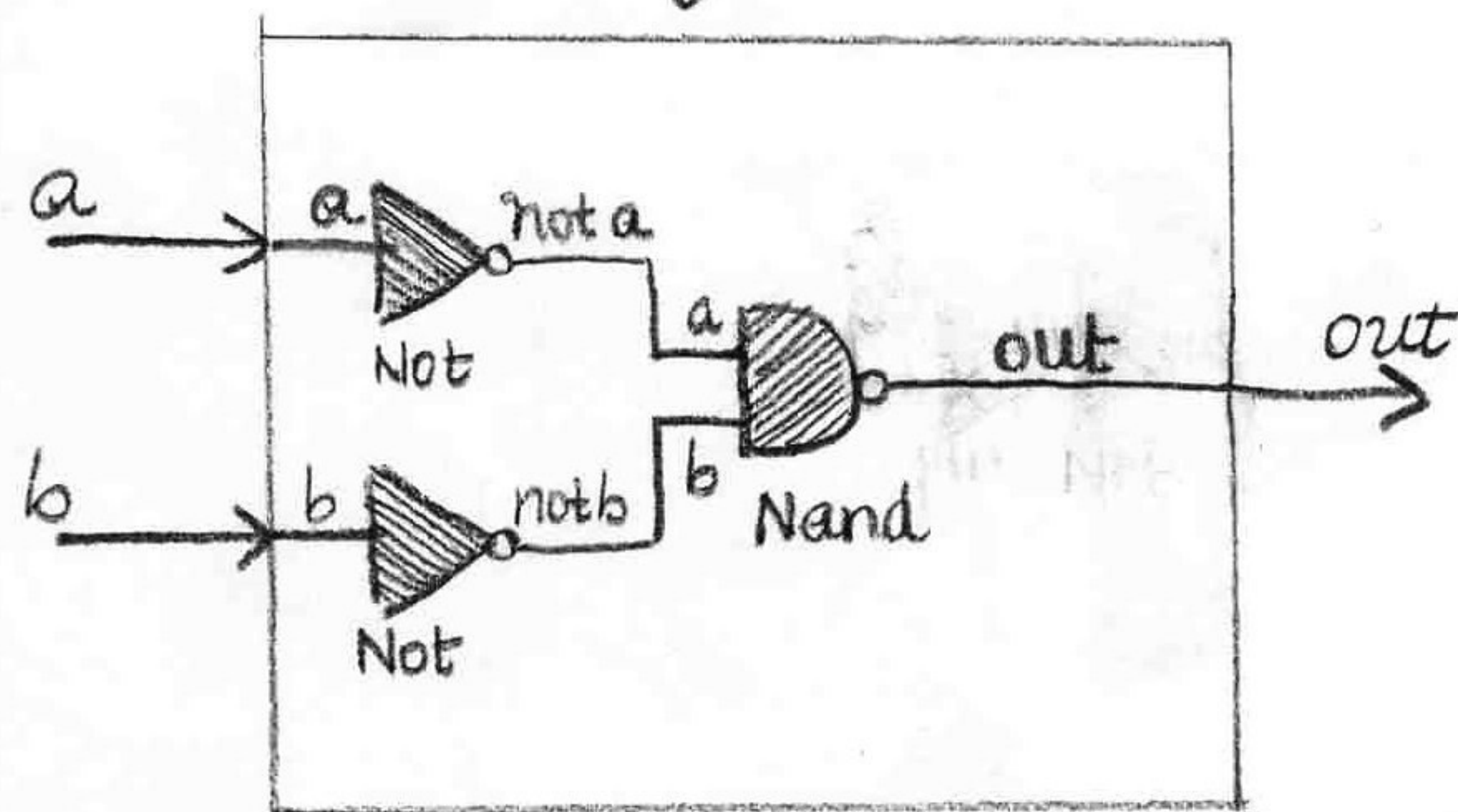

input - output

0	0	0
1	0	1
0	1	1
1	1	1

$$\text{Or}(a, b) = \text{Not}(\text{And}(\text{Not}(a), \text{Not}(b)))$$

Or {

IN a, b;  
OUT out;


Not(in=a, out=not a);

Not(in=b, out=not b);

Nand(a=not a, b=not b, out=out);

}

### Xor gate

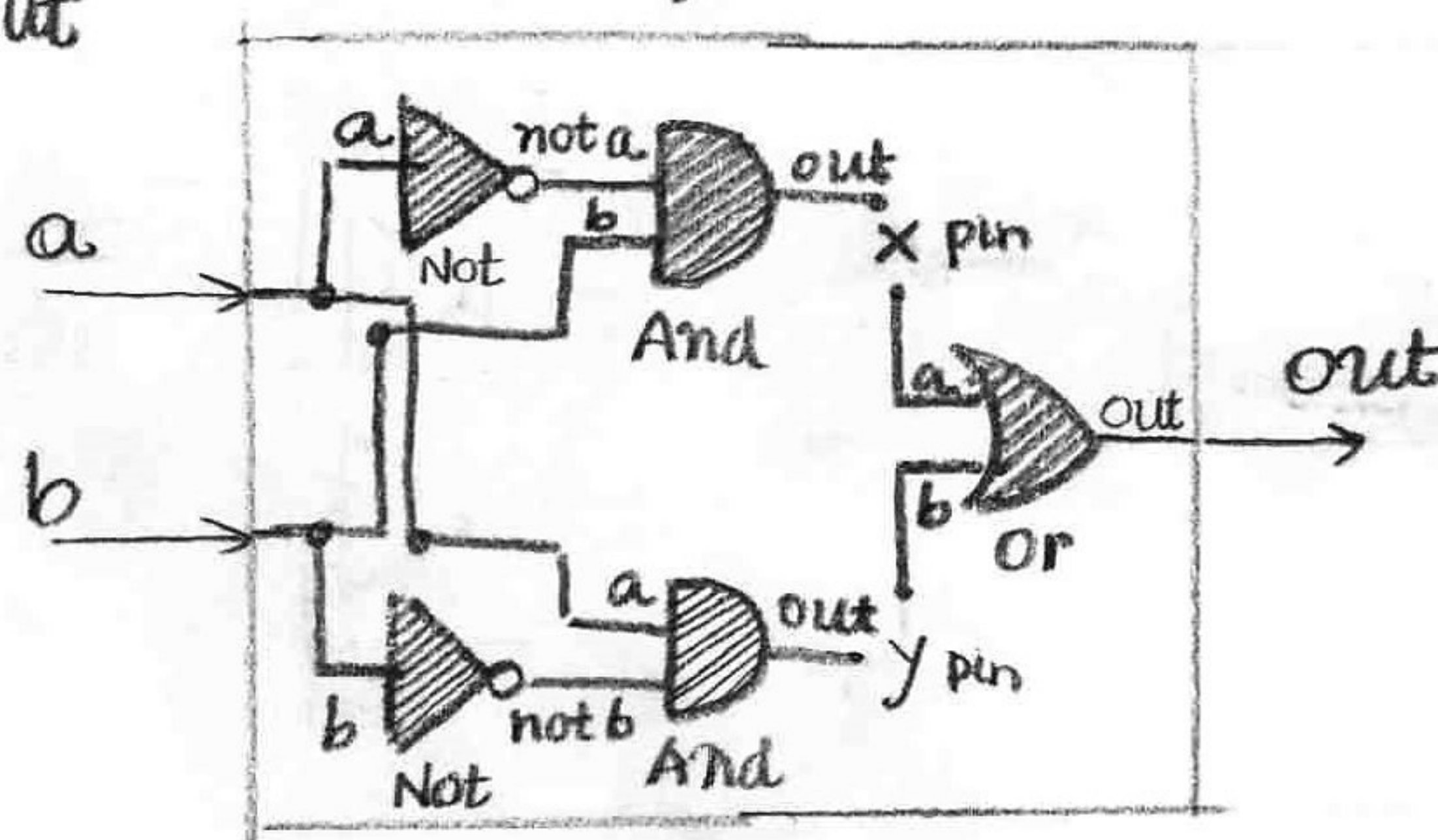

input - output

0	0	0
1	0	1
0	1	1
1	1	0

$$\text{Xor}(a, b) = \text{Or}(\text{And}(a, \text{Not}(b)), \text{And}(\text{Not}(a), b))$$

XOR {

IN a, b;  
OUT out;

Not(in=a, out=not a);

Not(in=b, out=not b);

And(a=a, b=not b, out=x);

And(a=not a, b=b, out=y);

Or(a=x, b=y, out=out);

}